

ISSUES AND DIRECTIONS IN IR DETECTOR
READOUT ELECTRONICS

Eric R. Fossum
Department of Electrical Engineering
Columbia University
New York, NY 10027

Abstract

An introduction to the major issues encountered in the read out of imaging detector arrays in the infrared will be presented. These include circuit issues such as multiplexing, buffering, and noise, as well as materials issues.

Future directions in infrared readout electronics will also be discussed. These include on-chip signal processing and advanced hybridization schemes. Finally, recent work at Columbia on 2DEG-CCDs for IR detector multiplexing will be described.

Issues in FPA Readout Electronics




Eric R. Fossum
Dept. of Electrical Engineering
Columbia University
NY NY 10027

ERF




Outline

1. Present Imager Readout Architectures
2. Special Problems in LWIR Readout
3. GaAs CCD Readout
4. On-chip Signal Processing


ERF

   

4-PHASE CHARGE TRANSFER

   

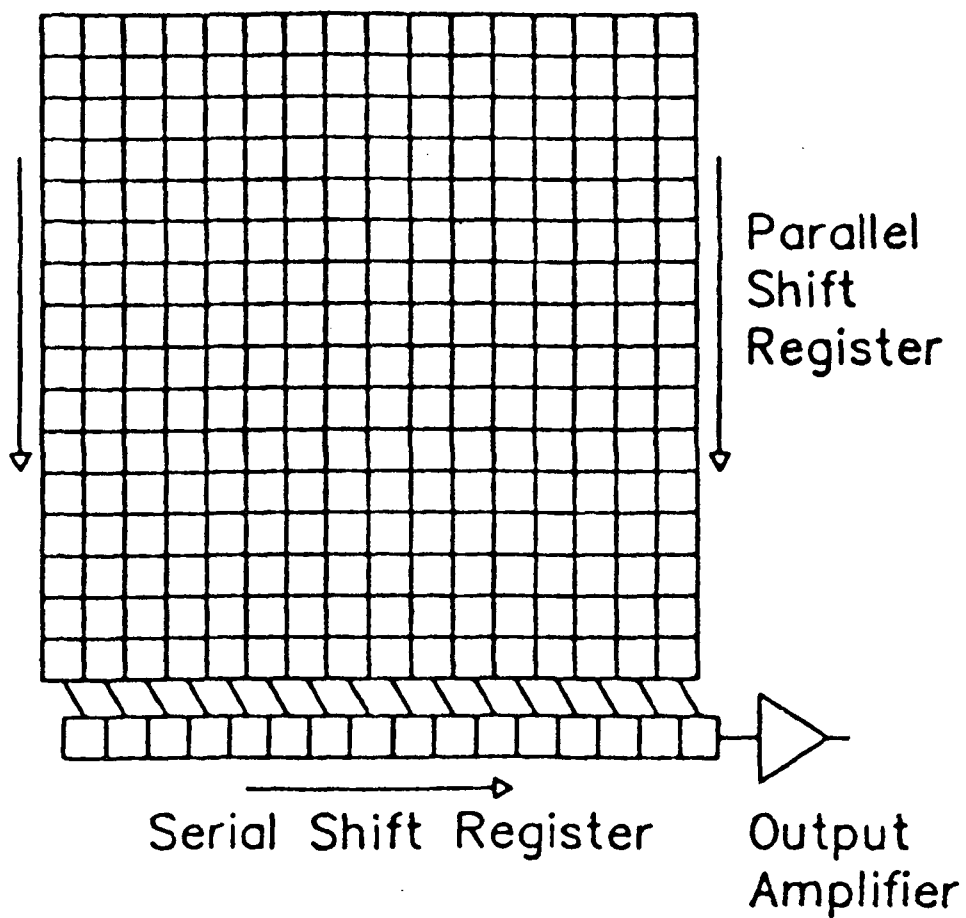Schematic illustration of a charge-coupled device (CCD) imager read-out structure.




COMMERCIALY-AVAILABLE CCDS


<u>MANUFACTURER</u>	<u>DEVICE</u>	<u>FORMAT</u>	<u>STRUCTURE</u>	<u>PIXEL SIZE, μm</u>	<u>DIMENSIONS, mm</u>	<u>GATES/PIXEL</u>
EG&G Reticon (US)	RA0256B	256x256	Full Frame	40x40	10.2x10.2	4
Fairchild (US)	CCD222	488x380	Interline	30x18	8.8x11.4	2
Photometrics (US)		516x516	Full Frame	20x20	10.3x10.3	4
Tektronix (US)	TK512M	512x512	Full Frame	27x27	13.8x13.8	3 Thinned
	TK2048M	2048x2048	Full Frame	27x27	55.3x55.3	3 Thinned, Develop.
Videk (US)	Megaplug	1320x1035	Full Frame	6.8x6.8	9.0x7.0	2
Amperex (Holland)	NKA1010	604x294	Frame Transfer	10x15.6		4/3
Dalsa (Canada)	IA-D1-0256	256x256	Frame Transfer	16x16	4.1x4.1	
Eng. Elec. Valve (UK)	P-86131	576x385	Full Frame	22x22	12.8x8.5	
Sanyo (Japan)		572x485				
		640x480				
Texas Inst. (Japan)	T1241	754x488	Frame Transfer	11.5x27		1
	TC215	1024x1024	Full Frame	12x12	12.3x12.3	1
	TC217	1134x486	Frame Transfer	7.8x13.6		1
Thomson CSF (France)	TNX31156	1024x1024	Full Frame	19x19	19.5x19.5	4 Develop.
	TNX7863	576x384	Full Frame	23x23		4
Toshiba (Japan)		1920x1036				

INTEGRATING INPUTS

1. DIRECT INJECTION

 

2. GATE MODULATION

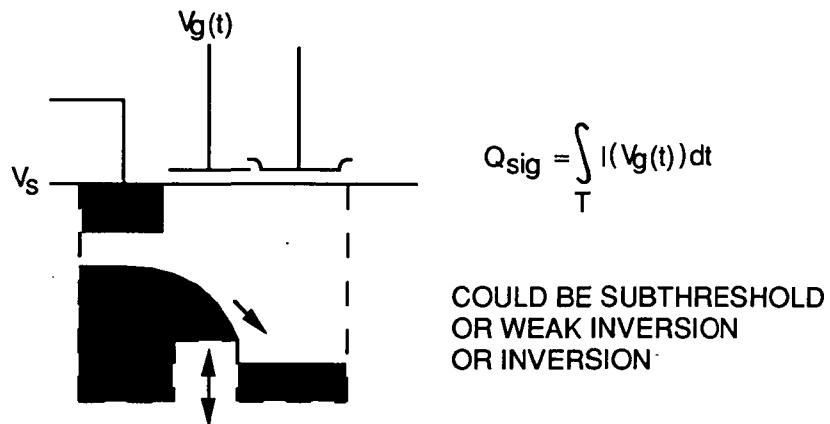

 


Fig. 5. Pixel cross section of 256 x 256 element IR-CCD image sensor.

 


Fig. 3. Schematic diagram of 256 x 256 element IR-CCD image sensor.

Kimata, et al. Opt. Eng 26(3) 211 (1987).

 


Fig. 2. Various detector readout structures: (a) gate readout (GRO); (b) gate-coupled readout (GCRO) to CCD; (c) direct-injection (DI) current readout; (d) direct-injection ancillary current (DIAC) readout; (e) direct-injection bipolar (DIB) current readout; (f) direct-injection bipolar ancillary current (DIBAC) readout; (g) buffered direct-injection (BDI) current readout.

Bluzer and Jensen Opt. Eng. 26(3) 241 (1987).

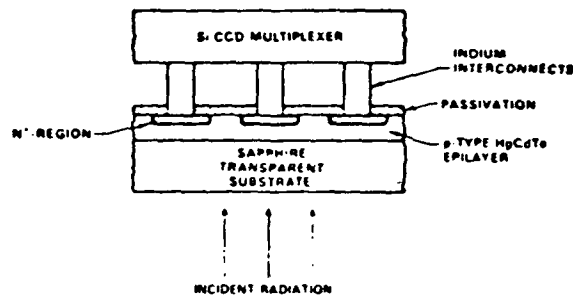
 


Fig. 8. Backside-illuminated hybrid FPA.

VURAL



 


Fig. 6. Direct-injection input circuit schematic for 64 x 64 multiplexer.

Comparison of CCD Technologies

 

Schematic illustration of a MOS-CCD imager read-out structure.

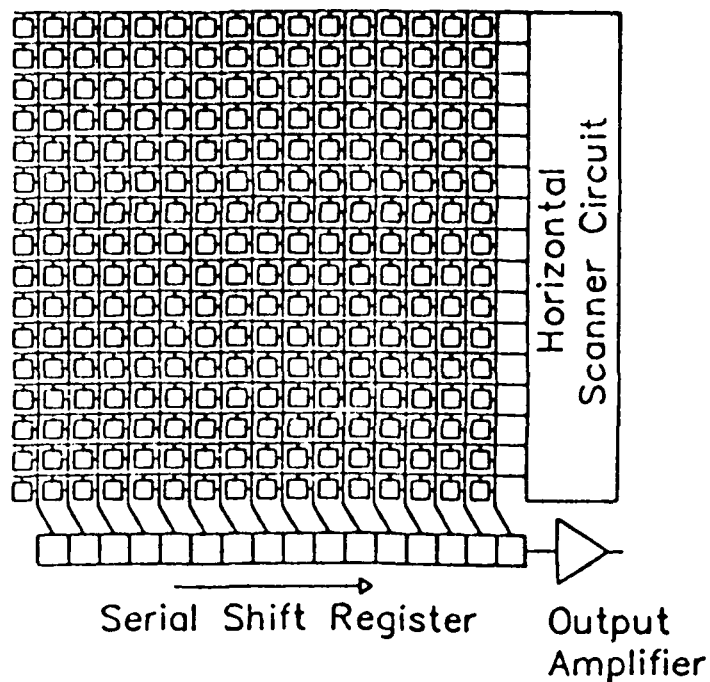

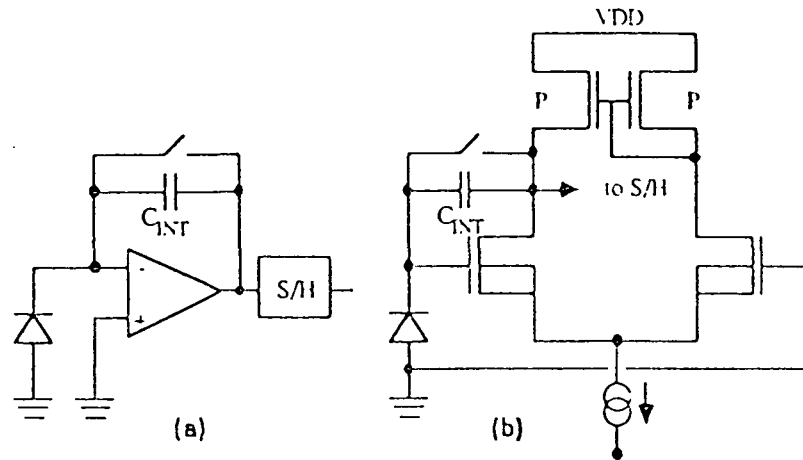


Fig. 5. Reset integrator input circuit: (a) functional block diagram, (b) MOSFET implementation.

 


Fig. 6. Buffered common gate input circuit: (a) functional block diagram, (b) MOSFET implementation.

Lockwood and Parrish, Opt. Eng 26(3) 228 (1987).

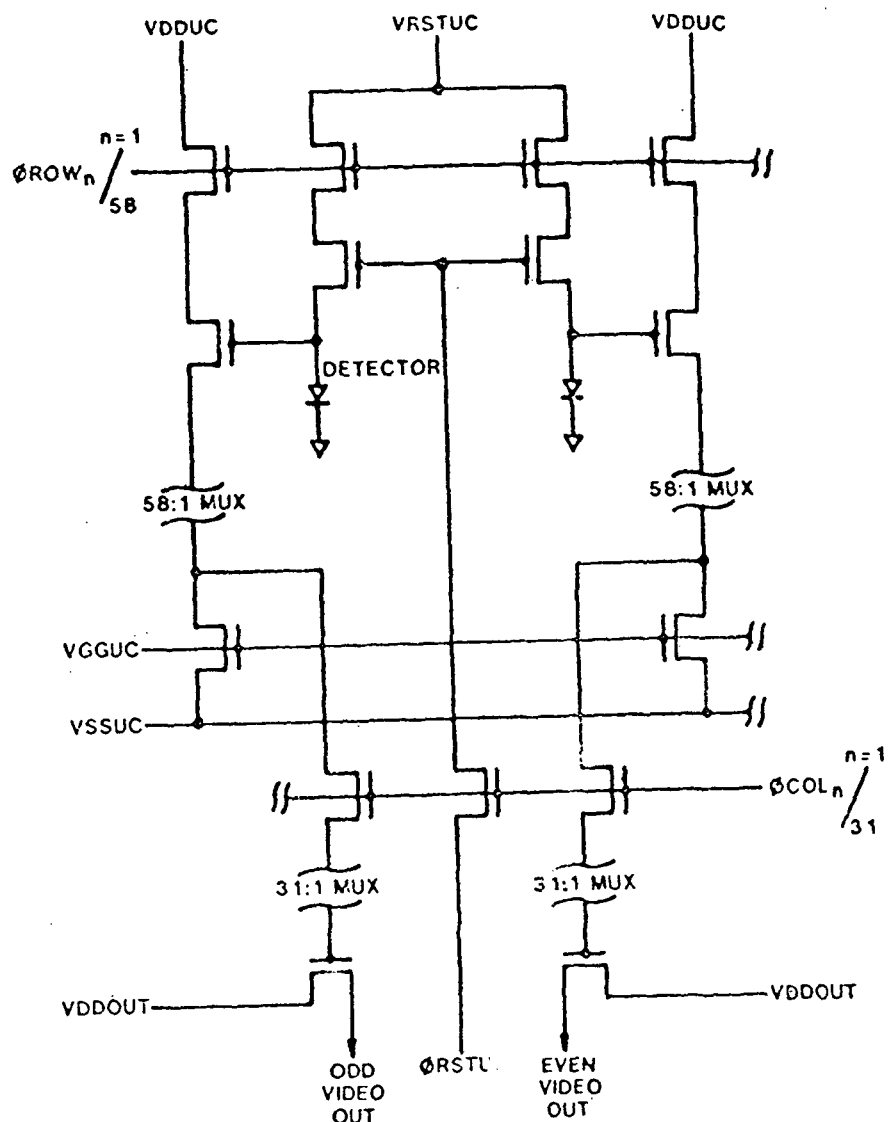


Fig. 2. Simplified schematic of the direct readout circuit used for this array.

 


Fig. 5. Representation of the voltage across a single pixel during an integration interval at the detector node.

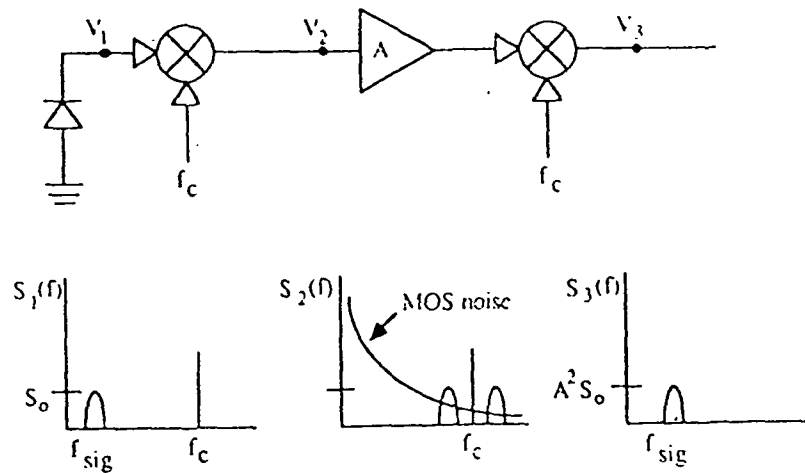


Fig. 8. Carrier modulation scheme used to upconvert detect signals to higher frequencies where MOSFET noise is low.

 


Fig. 9. Buffered common gate readout input circuit using chopper stabilization to reduce detector bias offsets and amplifier 1/f noise.

 


Fig. 10. Projected chopper-stabilized InSb focal plane performance.

Lockwood and Parrish, Opt. Eng 26(3) 228 (1987).

IMAGE ACQUISITION + IMAGE PROCESSING

FOCAL PLANE IMAGE PROCESSING

WHY

NOISE

DISTORTION

POWER

SIZE

RELIABILITY

COST


WHY NOT

YIELD



CHIP SIZE

COOLING

NON-UNIFORMITY CORRECTION

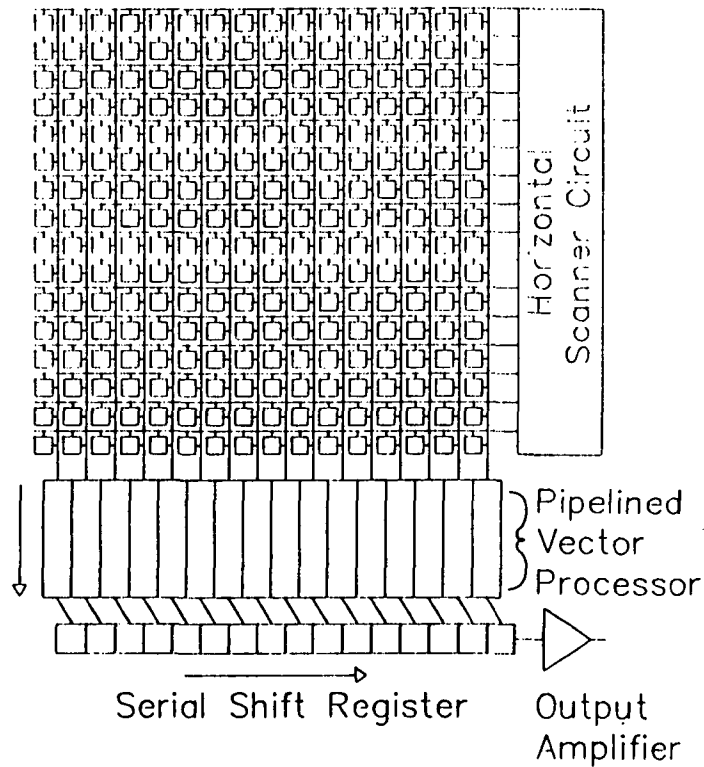

NON-UNIFORMITY CORRECTION

 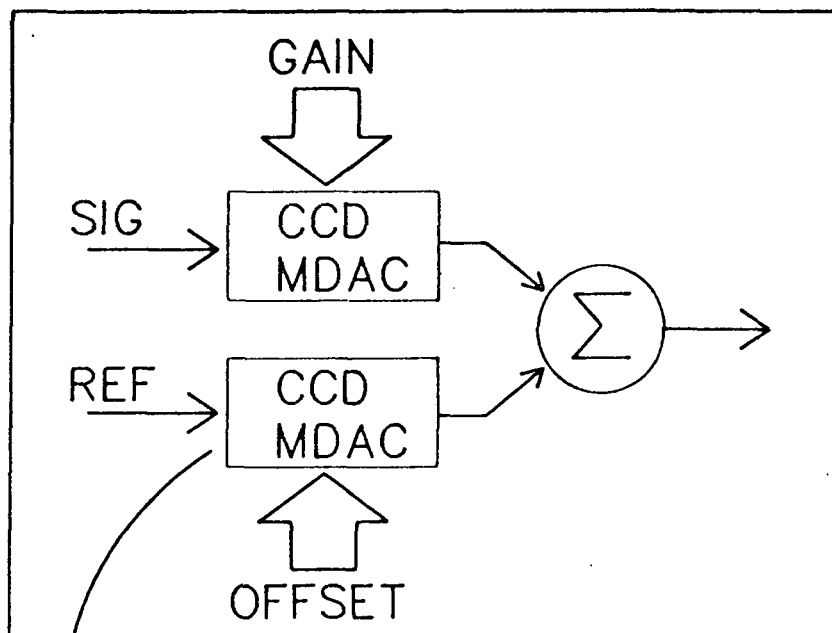

 
 


Fig. 2. Photograph of (a) serial recursive circuit and (b) single stage of pipeline circuit.

 


Fig. 3. Oscilloscope photograph showing analog output of pipeline programmable gain control circuit in response to a digital ramp (upper trace) and MSB of digital control word (lower trace).


 


Fig. 4. Differential linearity error of pipeline circuit. Note that 1 LSB tic mark corresponds to 1/1024 of full scale.

CCD Programmable Gain Control Circuit Performance Summary

	<u>Pipeline</u>	<u>Serial</u>
Technology	3 μ m CCD	3 μ m CCD
Circuit Size	0.4 mm ²	0.013 mm ²
Resolution	10 bits	variable
Integral Linearity	8 bits	6 bits
Differential Linearity	8 bits	6 bits
Clock Voltage	10 volts	10 volts
Bucket Cap. (electrons)	5x10 ⁶	5x10 ⁶
Power (10 ³ conv/sec)	2 μ W	2 μ W
Max. Conversion Rate	>8x10 ⁶ /sec	>0.5x10 ⁶ /sec

Spatially Parallel Architecture (SIMD)

 

FPA CCC POWER CONSIDERATIONS

TO TRANSFER 1 BUCKET (HALF FULL) $\Delta V = 10$ VOLTS

$$\text{ENERGY} = 8 \mu\text{J}$$

ARRAY WITH 1500 PEs OPERATING IN PARALLEL

$$12 \text{ nJ}$$

SAY EACH INSTRUCTION REQUIRES 10 TRANSFERS,
SAY 100 INSTRUCTIONS PER PIXEL TO PREPROCESS

$$12 \mu\text{J PER FRAME}$$

SAY 1000 Hz FRAME RATE*

12 mW CHIP DISSIPATION

ADD IN DRIVERS, PARASITICS, MULTIPLY BY 2

$$25 \text{ mW}$$

FOR 1 kHz REAL TIME PREPROCESSED IMAGERY

* AT 100 nsec/TRANSFER, CAN OPERATE AT 1MHz INSTRUCTION
RATE, OR 10 kHz FRAME RATE POSSIBLE

NOISE CONSIDERATIONS

SAY BIAS = 10 V \rightarrow 8 VOLT BUCKET

~250,000,000 ELECTRONS/HOLES

SAY WANT 8-BIT EQUIVALENT ACCURACY W/ SNR = 4 ON LSB

\rightarrow MAXIMUM NOISE ~ 250,000 CARRIERS

NOISE SOURCES:

1) CAPACITIVELY COUPLED CIRCUITS

$$n_{\text{RMS}} = \frac{(kTC)^{1/2}}{q} \lesssim 1000 \text{ CARRIERS}$$

2) TRANSFER

$$n_{\text{RMS}} = \frac{(2EN)^{1/2}}{0.05} \lesssim 5000 \text{ CARRIERS}$$

\swarrow FULL

3) INTERFACE


$$(1.4 kTD_{IT}A_E)^{1/2} \lesssim 200 \text{ CARRIERS}$$

CCC PROGRAM, SAY 50 TRANSFERS AND 10 FILL & SPILLS

\rightarrow RMS 35,000 CARRIERS

WHY GaAs CCDs ?


Device Structure

 


Features

- High Electron Mobility
 - High Transfer Speed
 - High f_t Transistors
- Wide Bandgap
 - Radiation Hard
 - Low Noise
- Semi-Insulating Substrate
 - Low Parasitic Capacitance
 - Mesa Isolation
- Compatibility with III-V Detectors


BAND DIAGRAM OF GaAs CCD

 



Without Signal Charge

 



With Signal Charge

 


Capacitive-Gate CCD

  


Resistive-Gate CCD

  


Silicon CCD

 


2DEG CCD

 


BAND DIAGRAM OF 2DEG CCD

 

Without Signal Charge

 


With Signal Charge

 

2DEG RGCCD

Device Structure

 

Features


- High Electron Mobility
 - High Transfer Speed
 - High Performance 2DEGFET
- Large Dynamic Range
 - $n_s > 1 \times 10^{12} / \text{cm}^2$
- High Sensitivity Input
- Enhanced
 - Low Temperature Performance

OPERATION OF 2DEG RGCCDs


Room Temperature

4 Phase Clocking, 32 Stages (128 Transfers)

 1 μm Electrode Width, 4 μm Spacing, 100 μm Channel Width



 Uniform-Doped 2DEG RGCCD
CTE = 0.999 At 1 GHz






Planar-Doped 2DEG RGCCD
CTE > 0.999 At 133 KHz

Advances in 2DEG CCDs


Year	Group	Channel Layer Material	Gate Structure	Gap Size	Gate Length x Width (μm)	Clock Frequency	CTE	Test Conditions
1982	Rockwell	AlGaAs /GaAs	Capacitive	2	40 x 400	< 83 KHz	0.98	300 K
1983	Rockwell	AlGaAs /GaAs	Capacitive	1	5 x	< 83 KHz	< 0.9	300 K
							0.989	77 K
1990	Columbia	AlGaAs /GaAs	Resistive	N/A	5 x 100	13 MHz - 1 GHz	0.999	300 K
1990	Columbia	AlGaAs /GaAs (δ -Doped)	Resistive	N/A	5 x 100	130 KHz - 1 GHz	> 0.999	300 K
1990	Columbia	InAlAs /InGaAs (δ -Doped)	Resistive	N/A	5 x 100			

DIRECT DETECTION

   


INDIRECT DETECTION

Direct Injection

 

INDIRECT DETECTION

Gate Modulation

 


GaAs CCD MULTIPLEXER DESIGN

- Linear Arrays (32 Stages, RGCCD, CGCCD)
 - Direct Detection
 - Indirect Detection
 - Direct Injection
 - Gate modulation
- 2-D Arrays (32x32, RGCCD)
 - Direct Detection

RESEARCH ISSUES

- Leakage Current Reduction
 - Transport Mechanisms
 - Materials Quality
 - Structure
- Dynamic Range
 - Pinch Off Voltage
 - Leakage Current
- New Material System (InAlAs/InGaAs)
 - Higher Electron Mobility
 - Larger Dynamic Range

Planar-Doped In Al As / In Ga As RGCCD

 

- High Mobility ($\sim 20,000 \frac{\text{cm}^2}{\text{Vs}}$ at 77 K)
- Large Sheet Carrier Density
- SWIR Direct Detection
- Compatible with Fiber-optic Integration

Present and Future Issues in Readout Electronics

Hybridization Technology

center-to-center spacing
array size
buttability
reliability

Multiplexer Material

thermal match
low $1/f$ noise devices

On-Chip Signal Processing

random event correction
detector non-uniformity correction
image processing
signature recognition

4/15/90 DRF